

main ▾

...

Digital-electronics-1 / Labs / 07-ffs / README.md



SimonCieslar Update README.md

🕒 History

👤 1 contributor

Raw

Blame



445 lines (363 sloc) | 12.6 KB

# Labs - 07 - Latches and Flip-flops

## Lab assignment

1. Preparation tasks (done before the lab at home). Submit:

- Characteristic equations and completed tables for D, JK, T flip-flops.

2. D latch. Submit:

- VHDL code listing of the process `p_d_latch` with syntax highlighting,
- Listing of VHDL reset and stimulus processes from the testbench `tb_d_latch.vhd` file with syntax highlighting and asserts,
- Screenshot with simulated time waveforms; always display all inputs and outputs. The full functionality of the entity must be verified.

3. Flip-flops. Submit:

- VHDL code listing of the processes `p_d_ff_arst`, `p_d_ff_rst`, `p_jk_ff_rst`, `p_t_ff_rst` with syntax highlighting,
- Listing of VHDL clock, reset and stimulus processes from the testbench files with syntax highlighting and asserts,
- Screenshot with simulated time waveforms; always display all inputs and outputs. The full functionality of the entities must be verified.

4. Shift register. Submit:

- Image of the shift register schematic. The image can be drawn on a computer or by hand.  
Name all inputs, outputs, components and internal signals.

## 1. Preparation tasks

### 1.1. Characteristic equations and completed tables for D, JK, T flip-flops

$$q_{n+1}^D = d$$

$$q_{n+1}^{JK} = j\bar{q}_n + \bar{k}q_n$$

$$q_{n+1}^T = t\bar{q}_n + \bar{t}q_n$$

clk	d	q(n)	q(n+1)	Comments
↑	0	0	0	No change
↑	0	1	0	Change
↑	1	1	1	No change
↑	1	0	1	Change

clk	j	k	q(n)	q(n+1)	Comments
↑	0	0	0	0	No change
↑	0	0	1	1	No change
↑	0	1	0	0	Reset
↑	0	1	1	0	Reset
↑	1	0	0	1	Set
↑	1	0	1	1	Set
↑	1	1	0	1	Toggle
↑	1	1	1	0	Toggle

clk	t	q(n)	q(n+1)	Comments
↑	0	0	0	No change

clk	t	q(n)	q(n+1)	Comments
↑	0	1	1	No change
↑	1	0	1	Invert
↑	1	1	0	Invert

## 2. D latch

---

### 2.1. VHDL code listing of the process `p_d_latch` with syntax highlighting

```
p_d_latch : process (d, arst, en)
begin
    if (arst = '1') then
        q      <= '0';
        q_bar <= '1';

        elsif (en = '1') then
            q      <= d;
            q_bar <= not d;
        end if;
    end process p_d_latch;
```

### 2.2. Listing of VHDL reset and stimulus processes from the testbench `tb_d_latch.vhd` file with syntax highlighting and asserts

```
p_stimulus : process
begin
    report "Stimulus process started" severity note;
    s_d <= '0';
    s_en <= '0';

    assert(s_q = '0')
    report "Error" severity error;

    --d sekv
    wait for 10 ns;
    s_d <= '1';
    wait for 10 ns;
    s_d <= '0';
    wait for 10 ns;
    s_d <= '1';
    wait for 10 ns;
    s_d <= '0';
    wait for 10 ns;
    s_d <= '1';
    wait for 10 ns;
    s_d <= '0';
```

```

--/d sekv

assert(s_q = '0' and s_q_bar = '1')
report "Error" severity error;

s_en <= '1';

--d sekv
wait for 10 ns;
s_d <= '1';
wait for 10 ns;
s_d <= '0';
wait for 10 ns;
s_d <= '1';
wait for 10 ns;
s_d <= '0';
wait for 10 ns;
s_d <= '1';
wait for 10 ns;
s_en <= '0'; -- en to 0
wait for 200 ns;
s_d <= '0';
--/d sekv


--d sekv
wait for 10 ns;
s_d <= '1';
wait for 10 ns;
s_d <= '0';
wait for 10 ns;
s_d <= '1';
wait for 10 ns;
s_d <= '0';
wait for 10 ns;
s_d <= '1';
wait for 10 ns;
s_d <= '0';
--/d sekv

--d sekv
wait for 10 ns;
s_d <= '1';
wait for 10 ns;
s_d <= '0';
wait for 10 ns;
s_d <= '1';
wait for 10 ns;
s_d <= '0';
wait for 10 ns;
s_d <= '1';
wait for 10 ns;
s_d <= '0';
--/d sekv

report "Stimulus process finished" severity note;
wait;
end process p_stimulus;

```
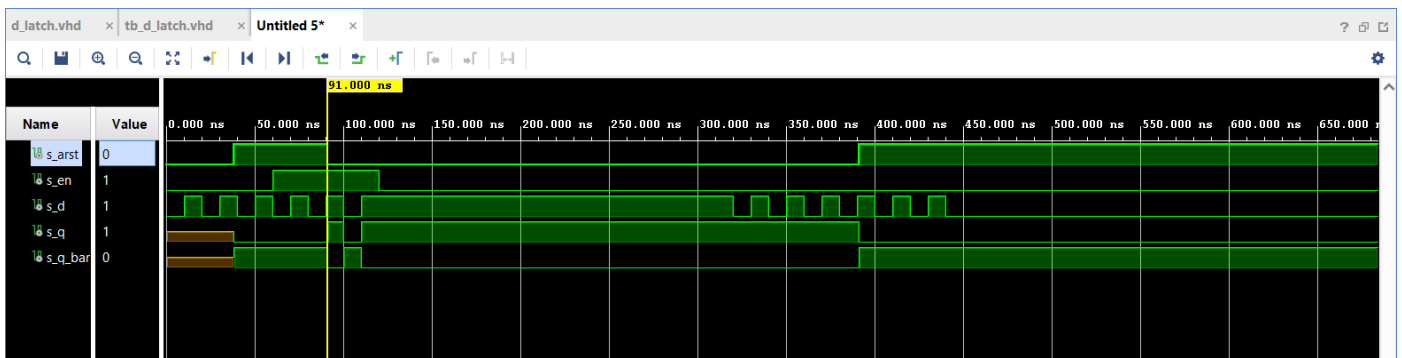
## 2.3. Screenshot with simulated time waveforms; always display all inputs and outputs. The full functionality of the entity must be verified



## 3. Flip-flops

### 3.1. VHDL code listing of the processes p\_d\_ff\_arst , p\_d\_ff\_rst , p\_jk\_ff\_rst , p\_t\_ff\_rst with syntax highlighting

Process p\_d\_ff\_arst

```
p_d_ff_arst : process (clk, arst)
begin
    if (arst = '1') then
        q      <= '0';
        q_bar <= '1';

    elsif rising_edge(clk) then
        q      <= d;
        q_bar <= not d;
    end if;
end process p_d_ff_arst;
```

Process p\_d\_ff\_rst

```
p_d_ff_rst : process (clk)
begin
    if rising_edge(clk) then
        if (rst = '1') then
            q      <= '0';
            q_bar <= '1';
        else
            q      <= d;
            q_bar <= not d;
        end if;
    end if;
end process p_d_ff_rst;
```

Process p\_jk\_ff\_rst

```

p_jk_ff_rst : process (clk)
begin
    if rising_edge(clk) then
        if (rst = '1') then
            s_q <= '0';
        else
            if (j = '0' and k = '0') then
                s_q <= s_q;

            elsif (j = '0' and k = '1') then
                s_q <= '0';

            elsif (j = '1' and k = '0') then
                s_q <= '1';

            elsif (j = '1' and k = '1') then
                s_q <= not s_q;

            end if;
        end if;
    end if;
end process p_jk_ff_rst;

q      <= s_q;
q_bar <= not s_q;

```

Process p\_t\_ff\_rst

```

p_t_ff_rst : process (clk)
begin
    if rising_edge(clk) then
        if (rst = '1') then
            s_q      <= '0';
            s_q_bar <= '1';
        else
            if (t = '0') then
                s_q      <= s_q;
                s_q_bar <= s_q_bar;
            else
                s_q      <= not s_q;
                s_q_bar <= not s_q_bar;
            end if;
        end if;
    end if;
end process p_t_ff_rst;

q      <= s_q;
q_bar <= s_q_bar;

```

### 3.2. Listing of VHDL clock, reset and stimulus processes from the testbench files with syntax highlighting and asserts

## Stimulus process from the testbench tb\_d\_ff\_arst

```
p_stimulus : process
begin
    report "Stimulus process started" severity note;
    s_d <= '0';

    --d sekv
    wait for 14 ns;
    s_d <= '1';
    wait for 10 ns;
    s_d <= '0';

    wait for 6 ns;
--    assert()
--    report "";

    wait for 4 ns;
    s_d <= '1';
    wait for 10 ns;
    s_d <= '0';
    wait for 10 ns;
    s_d <= '1';
    wait for 10 ns;
    s_d <= '0';
    --/d sekv

    --d sekv
    wait for 10 ns;
    s_d <= '1';
    wait for 10 ns;
    s_d <= '0';
    wait for 10 ns;
    s_d <= '1';
    wait for 10 ns;
    s_d <= '0';
    wait for 10 ns;
    s_d <= '1';
    wait for 10 ns;
    s_d <= '0';
    --/d sekv

    report "Stimulus process finished" severity note;
    wait;
end process p_stimulus;
```

## Stimulus process from the testbench tb\_d\_ff\_rst

```
p_stimulus : process
begin
    report "Stimulus process started" severity note;
    s_d <= '1';

    --d sekv
```

```

wait for 10 ns;
s_d <= '0';
wait for 10 ns;
s_d <= '1';
wait for 10 ns;
s_d <= '0';
wait for 10 ns;

assert(s_q = '0' and s_q_bar = '1')
report "Error - Failed" severity error;

wait for 20 ns;
s_d <= '1';
wait for 25 ns;

assert(s_q = '1' and s_q_bar = '0')
report "Error - Failed" severity error;
--/d sekv

--d sekv
wait for 10 ns;
s_d <= '0';
wait for 10 ns;
s_d <= '1';
wait for 10 ns;
s_d <= '0';
wait for 10 ns;
s_d <= '1';
wait for 10 ns;
s_d <= '0';
wait for 10 ns;
s_d <= '1';
--/d sekv

report "Stimulus process finished" severity note;
wait;
end process p_stimulus;

```

Stimulus process from the testbench tb\_jk\_ff\_rst

```

p_stimulus : process
begin
    report "Stimulus process started" severity note;
    s_j <= '0';
    s_k <= '0';

    --d sekv
    wait for 37 ns;
    s_j <= '0';
    s_k <= '0';
    wait for 3 ns;
    s_j <= '1';
    s_k <= '0';
    wait for 7 ns;
    s_j <= '0';

```



```

s_k <= '1';
wait for 14 ns;
s_j <= '1';
s_k <= '0';
wait for 7 ns;
s_j <= '1';
s_k <= '1';
--/d sekv

--d sekv
wait for 7 ns;
s_j <= '0';
s_k <= '0';
wait for 7 ns;
s_j <= '0';
s_k <= '1';
wait for 7 ns;
s_j <= '1';
s_k <= '0';
wait for 7 ns;
s_j <= '1';
s_k <= '1';
--/d sekv

report "Stimulus process finished" severity note;
wait;
end process p_stimulus;

```

Stimulus process from the testbench tb\_t\_ff\_rst

```

p_stimulus : process
begin
    report "Stimulus process started" severity note;

    wait for 20 ns;
    s_t <= '1';
    wait for 10 ns;
    s_t <= '0';
    wait for 10 ns;
    s_t <= '1';
    wait for 10 ns;
    s_t <= '0';
    wait for 10 ns;
    s_t <= '1';
    wait for 10 ns;
    s_t <= '0';


    assert(s_q='1' and s_q_bar = '0')
    report "Error" severity error;

    report "Stimulus process finished" severity note;
    wait;
end process p_stimulus;


```

### 3.3. Screenshot with simulated time waveforms; always display all inputs and outputs. The full functionality of the entities must be verified


Waveform for d\_ff\_arst

 


Waveform for d\_ff\_rst

 

Waveform for jk\_ff\_rst

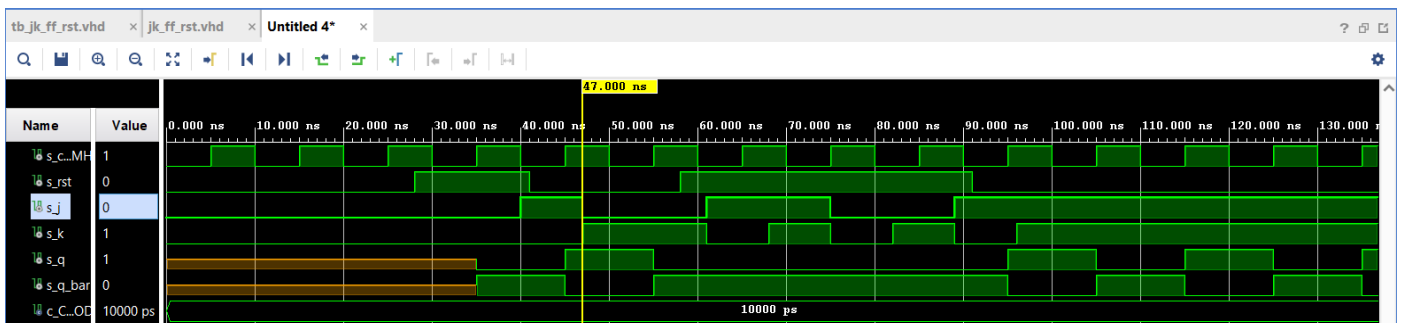

Waveform for t\_ff\_rst

 

## 4. Shift register

4.1. Image of the shift register schematic. The image can be drawn on a computer or by hand. Name all inputs, outputs, components and internal signals

Shift\_register

