

🔗 main ▾

...

[Digital-electronics-1](#) / [Labs](#) / [06-display\\_driver](#) / [README.md](#)

SimonCieslar Update README.md

🕒 History

👤 1 contributor

Raw

Blame



280 lines (220 sloc) | 8.46 KB

# Labs - 06 - Display\_driver

## Experiments on your own

1. On your smartphone, set slow motion video recording and observe the seven-segment display behavior:)
2. Extend the duration of one symbol on the 7-segment display ie. generic `g_MAX` in `driver_7seg_4digit.vhd` file and experimentally determine the maximum value at which switching by the human eye is not yet observable.
3. Design the structure of `driver_7seg_8digits` module, which controls all eight 7-segment displays.

## Lab assignment

1. Preparation tasks (done before the lab at home). Submit:
  - Timing diagram figure for displaying value 3.142 .
2. Display driver. Submit:
  - Listing of VHDL code of the process `p_mux` with syntax highlighting.
  - Listing of VHDL testbench file `tb_driver_7seg_4digits` with syntax highlighting and asserts,
  - Screenshot with simulated time waveforms; always display all inputs and outputs,


- Listing of VHDL architecture of the top layer.

### 3. Eight-digit driver. Submit:

- Image of the driver schematic. The image can be drawn on a computer or by hand.

## 1. Preparation tasks
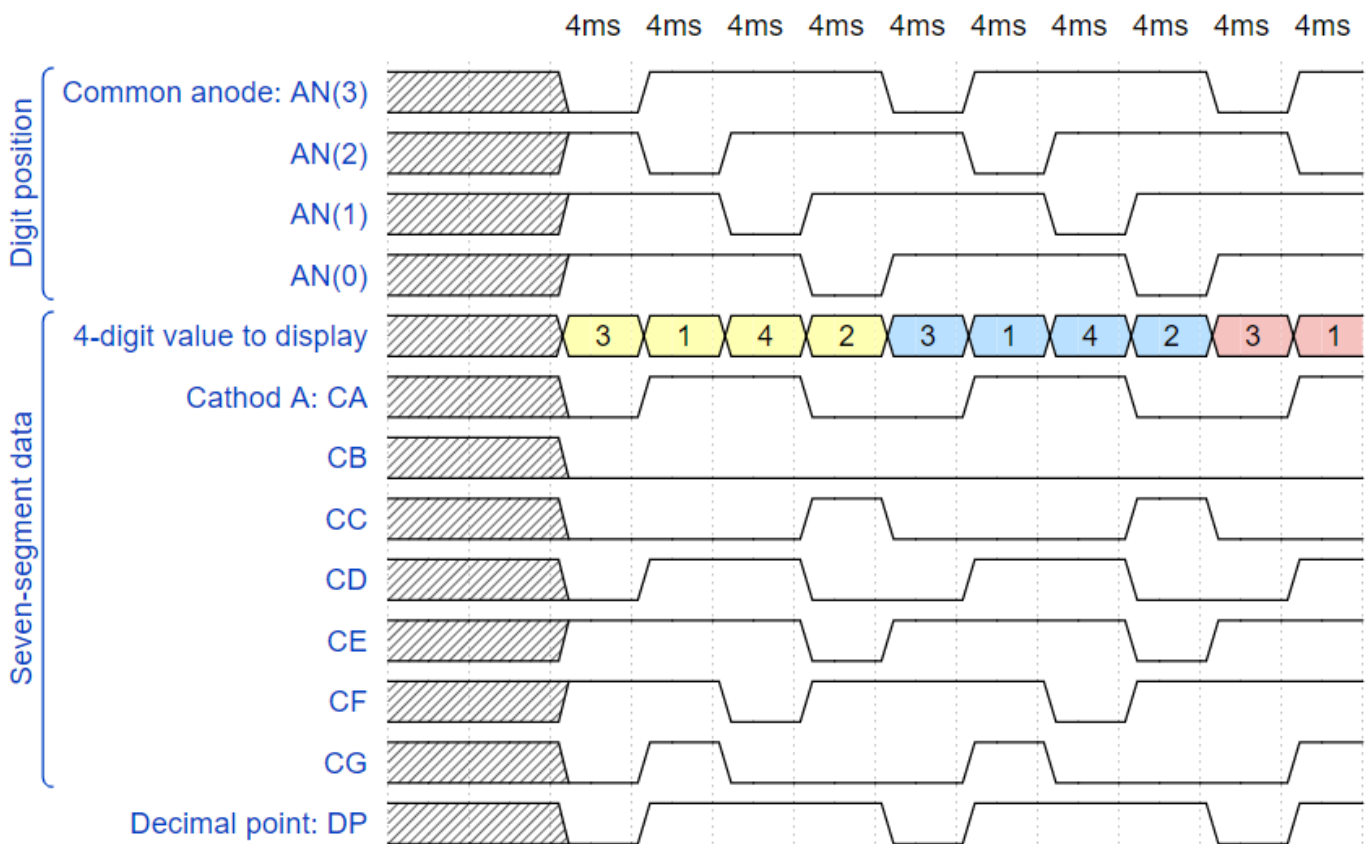
### 1.1. Timing diagram figure for displaying value 3.142



```
{
  signal:
  [
    ['Digit position',
      {name: 'Common anode: AN(3)', wave: 'xx01..01..01'},
      {name: 'AN(2)', wave: 'xx1'},
      {name: 'AN(1)', wave: 'xx1'},
      {name: 'AN(0)', wave: 'xx1'},
    ],
    ['Seven-segment data',
      {name: '4-digit value to display', wave: 'xx3333555599', data: ['3','1','4','2','3','1','4','2','3','1'],
      {name: 'Cathod A: CA', wave: 'xx01.0.1.0.1'},
      {name: 'CB', wave: 'xx0'},
      {name: 'CC', wave: 'xx0'},
      {name: 'CD', wave: 'xx0'},
      {name: 'CE', wave: 'xx1'},
      {name: 'CF', wave: 'xx1'},
      {name: 'CG', wave: 'xx0'},
    ],
    {name: 'Decimal point: DP', wave: 'xx01..01..01'},
  ],
}
```

```

],
head:
{
  text: '
                                4ms    4ms    4ms    4ms    4ms    4ms    4ms    4ms    4ms    4ms',
},
}

```

## 2. Display driver

### 2.1. Listing of VHDL code of the process `p_mux` with syntax highlighting

```

p_mux : process(s_cnt, data0_i, data1_i, data2_i, data3_i, dp_i)
begin
  case s_cnt is
    when "11" =>
      s_hex <= data3_i;
      dp_o  <= dp_i(3);
      dig_o <= "0111";

    when "10" =>
      s_hex <= data2_i;
      dp_o  <= dp_i(2);
      dig_o <= "1011";

    when "01" =>
      s_hex <= data1_i;
      dp_o  <= dp_i(1);
      dig_o <= "1101";

    when others =>
      s_hex <= data0_i;
      dp_o  <= dp_i(0);
      dig_o <= "1110";
  end case;
end process p_mux;

```

### 2.2. Listing of VHDL testbench file `tb_driver_7seg_4digits` with syntax highlighting and asserts

```

-----
--
-- Template for 4-digit 7-segment display driver testbench.
-- Nexys A7-50T, Vivado v2020.1.1, EDA Playground
--
-- Copyright (c) 2020 Tomas Fryza
-- Dept. of Radio Electronics, Brno University of Technology, Czechia
-- This work is licensed under the terms of the MIT license.
--
-----

```

```

library ieee;
use ieee.std_logic_1164.all;

-----
-- Entity declaration for testbench
-----

entity tb_driver_7seg_4digits is
    -- Entity of testbench is always empty
end entity tb_driver_7seg_4digits;

-----
-- Architecture body for testbench
-----

architecture testbench of tb_driver_7seg_4digits is

    -- Local constants
    constant c_CLK_100MHZ_PERIOD : time      := 10 ns;

    --Local signals
    signal s_clk_100MHz : std_logic;
    --- WRITE YOUR CODE HERE
    signal s_reset : std_logic;

    signal s_data0 : std_logic_vector(4 - 1 downto 0);
    signal s_data1 : std_logic_vector(4 - 1 downto 0);
    signal s_data2 : std_logic_vector(4 - 1 downto 0);
    signal s_data3 : std_logic_vector(4 - 1 downto 0);

    signal s_dp_i   : std_logic_vector(4 - 1 downto 0);
    signal s_dp_o   : std_logic;
    signal s_seg    : std_logic_vector(7 - 1 downto 0);

    signal s_dig    : std_logic_vector(4 - 1 downto 0);

begin
    -- Connecting testbench signals with driver_7seg_4digits entity
    -- (Unit Under Test)
    uut_driver_7seg_4digits : entity work.driver_7seg_4digits
    port map (
        clk => s_clk_100Mhz,
        reset => s_reset,

        data0_i => s_data0,
        data1_i => s_data1,
        data2_i => s_data2,
        data3_i => s_data3,

        dp_i => s_dp_i,

        dp_o => s_dp_o,
        seg_o => s_seg,
        dig_o => s_dig
    );
    -----
    -- Clock generation process

```

```

-----
p_clk_gen : process
begin
    while now < 750 ns loop          -- 75 periods of 100MHz clock
        s_clk_100MHz <= '0';
        wait for c_CLK_100MHZ_PERIOD / 2;
        s_clk_100MHz <= '1';
        wait for c_CLK_100MHZ_PERIOD / 2;
    end loop;
    wait;
end process p_clk_gen;

```

```

-----
-- Reset generation process
-----

```

```

p_reset_gen : process
begin
    s_reset <= '0';
    wait for 28 ns;

    -- Reset activated
    s_reset <= '1';
    wait for 53 ns;

    -- Reset deactivated
    s_reset <= '0';
    wait for 660 ns;

end process p_reset_gen;

```

```

-----
-- Data generation process
-----

```

```

p_stimulus : process
begin
    report "Stimulus process started" severity note;
    -- 3.142
    s_data3 <= "0011";
    s_data2 <= "0001";
    s_data1 <= "0100";
    s_data0 <= "0010";

    s_dp_i <= "0111";

    --wait for 350 ns;



    --s_data3 <= "0001";
    --s_data2 <= "0000";
    --s_data1 <= "0001";
    --s_data0 <= "0000";

    report "Stimulus process finished" severity note;
    wait;
end process p_stimulus;

```

```
end architecture testbench;
```
 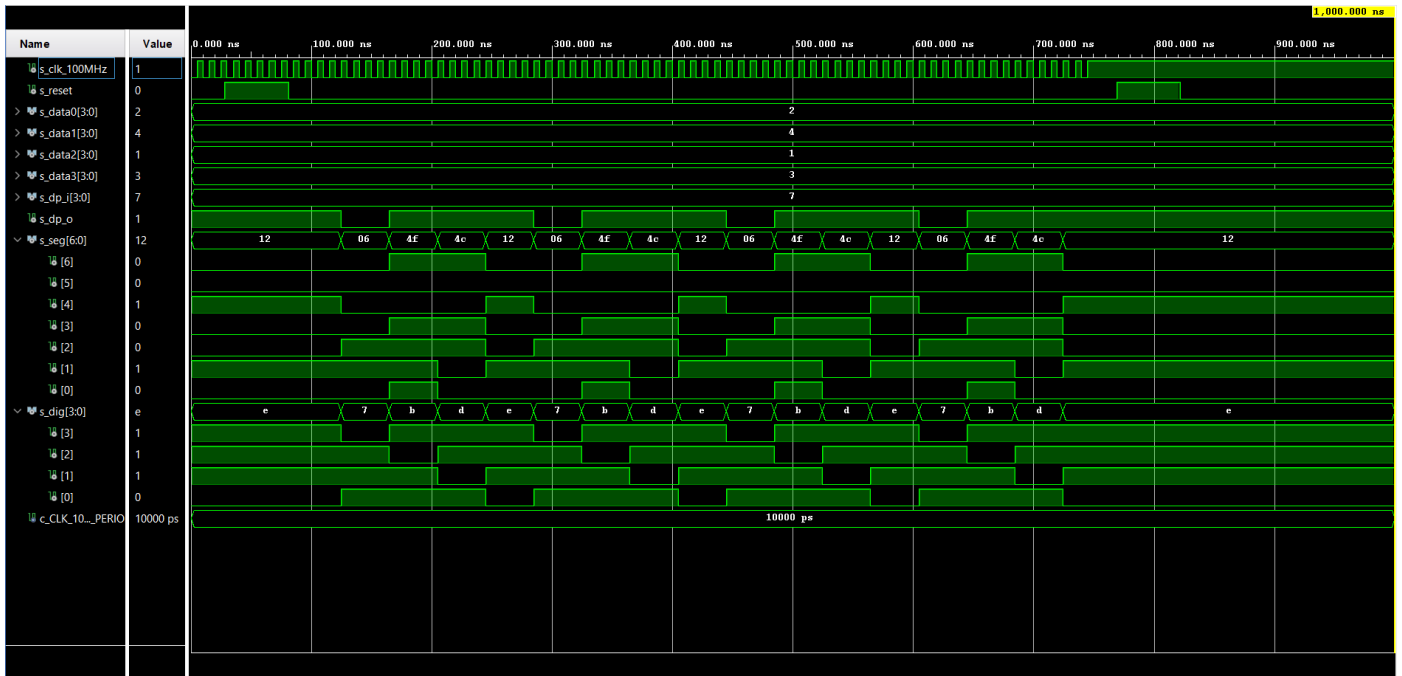
## 2.3. Screenshot with simulated time waveforms; always display all inputs and outputs



## 2.4. Listing of VHDL architecture of the top layer

```
architecture Behavioral of top is
begin
```

```
-- Instance (copy) of driver_7seg_4digits entity
```

```
driver_seg_4 : entity work.driver_7seg_4digits
```

```
port map
```

```
(
```

```
    clk          => CLK100MHZ,
```

```

reset      => BTNC,

data0_i(3) => SW(3),
data0_i(2) => SW(2),
data0_i(1) => SW(1),
data0_i(0) => SW(0),

data1_i(3) => SW(7),
data1_i(2) => SW(6),
data1_i(1) => SW(5),
data1_i(0) => SW(4),

data2_i(3) => SW(11),
data2_i(2) => SW(10),
data2_i(1) => SW(9),
data2_i(0) => SW(8),

data3_i(3) => SW(15),
data3_i(2) => SW(14),
data3_i(1) => SW(13),
data3_i(0) => SW(12),

seg_o(6)   => CA,
seg_o(5)   => CB,
seg_o(4)   => CC,
seg_o(3)   => CD,
seg_o(2)   => CE,
seg_o(1)   => CF,
seg_o(0)   => CG,

dig_o      => AN(4 - 1 downto 0),

dp_i       => "0111",
dp_o       => DP
);
end architecture Behavioral;

```

## 3. Eight-digit driver

---

### 3.1. Image of the driver schematic

# driver\_7seg\_8digits

