

main ▾

...

Digital-electronics-1 / Labs / Project / README.md



SimonCieslar Update README.md

🕒 History

👤 1 contributor

☰ 1050 lines (854 sloc) | 40.9 KB

...

# VHDL PROJECT - Parking assistant

## Team members

This project was created by Tereza Beránková, Samuel Blecha, Kryštof Buroň, Šimon Cieslar & Zuzana Czelová

[Tereza Beránková](https://github.com/xberan49/Digital-electronics-1/tree/main/Labs/Project) - <https://github.com/xberan49/Digital-electronics-1/tree/main/Labs/Project>

[Samuel Blecha](https://github.com/SamuelBlecha/Digital-electronics-1/tree/main/Labs/Project) - <https://github.com/SamuelBlecha/Digital-electronics-1/tree/main/Labs/Project>

[Kryštof Buroň](https://github.com/christ-0ff/Digital-Electronics-1/tree/main/Labs/project) - <https://github.com/christ-0ff/Digital-Electronics-1/tree/main/Labs/project>

[Šimon Cieslar](https://github.com/SimonCieslar/Digital-electronics-1/tree/main/Labs/Project) - <https://github.com/SimonCieslar/Digital-electronics-1/tree/main/Labs/Project>

[Zuzana Czelová](https://github.com/Zuzanaczm/Digital-electronics-1/tree/main/Labs/project) - <https://github.com/Zuzanaczm/Digital-electronics-1/tree/main/Labs/project>


## Project objectives

Our aim was to made parking assistant with HC-SR04 ultrasonic sensor, sound signaling using PWM, signaling by LED bargraph.
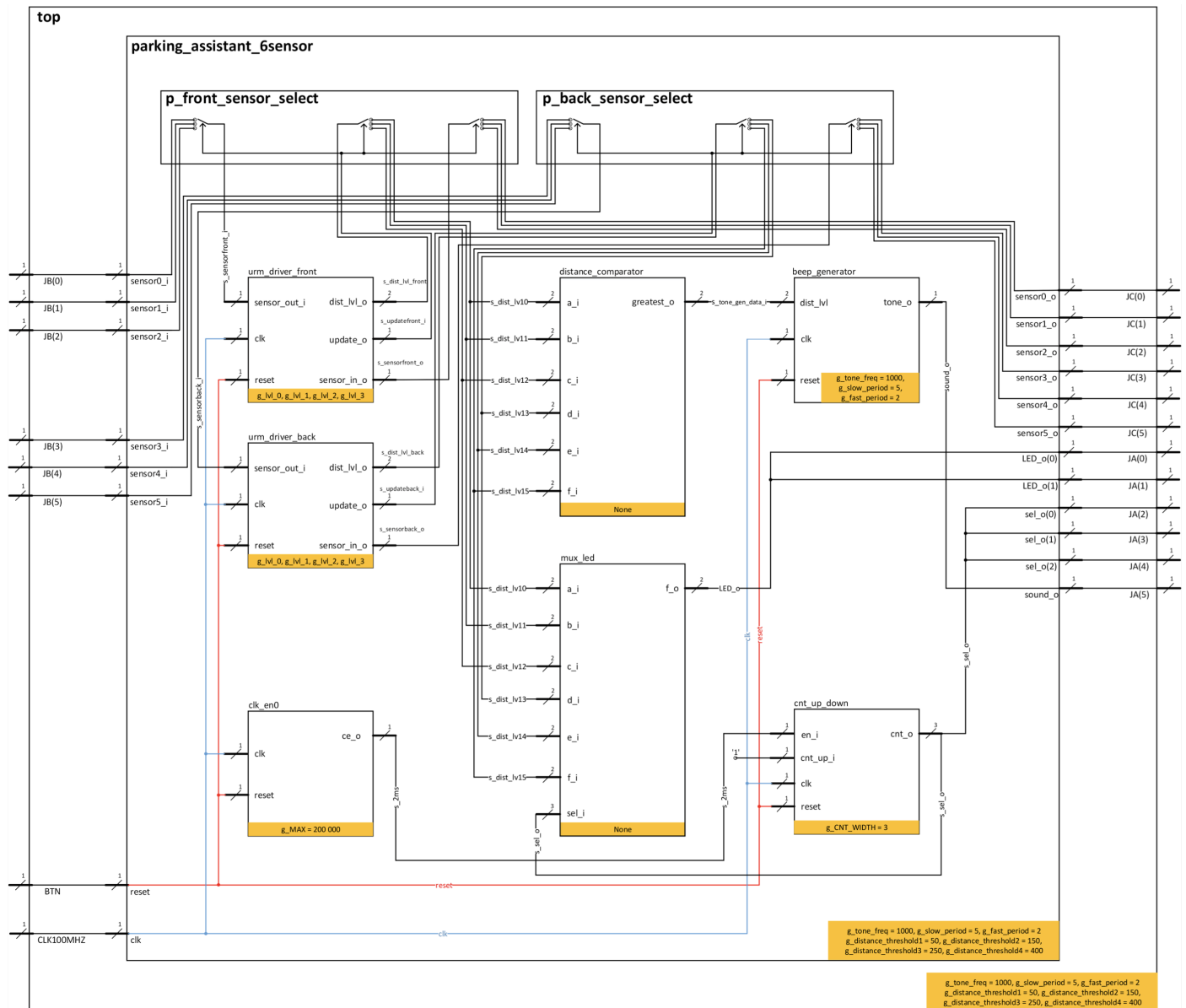
## Hardware description

The project is about parking assistant with 6 sensors (3 in front & 3 at the back). It measures distance in the front side and the back side - these sides measure at the same time and the sensors are switching among left, center and right side, but only one sensor works so they do not interfere each other. Distance, which is detected by each sensor, is signalized with LED bargraph. For every gained distance by sensors, there is also tone signalization that makes sound of "beep beep" when the closest target is present.

The description of hardware is pictured in the block diagram.



If you want to see original file of this diagram, you can find Project\_PS.pdf file in this project folder...

## VHDL design for parking assistant

### 1.Park assistant

#### A)Process of VHDL design

This process changes internal signals connections of `parking_assistant_6sensor` and sensors connected to it, so only one sensor detects distance at the time. We start with sensor on the left side - its input & output connects to internal signals of design source `parking_assistant_6sensor`. These internal signals are connected to `urm_driver_decoder`. After receiving an update from `urm_driver_decoder`, measured distance is saved to particular variable called `s_dist_lvl` that is defined for each sensor. The next state follows and the internal signals will be switched to input & output of the next sensor. Both processes (`p_front_sensor_select`; `p_back_sensor_select`) work the same but independently.

```
-----
-- Proces for switching between Left & Center & Right front sensor
-- So only one is measuring at the moment
-----
p_front_sensor_select : process(clk)
begin
    if rising_edge(clk) then
        if (reset = '1') then
            s_sensor_front <= LEFT; -- Initial state
        else
            case s_sensor_front is

                when LEFT =>
                    s_sensorfront_i <= sensor0_i;           -- Connecting input and output
                    sensor0_o <= s_sensorfront_o;           -- to its proper sensor input

                    if(s_updatefront_i = '1') then          -- Reciving update signal will
                        s_dist_lvl0 <= s_dist_lvl_front;    -- Save measured value to prop
                        s_sensor_front <= CENTER;            -- Change state.
                    end if;                                  -- Rest works same, but with i

                when CENTER =>
                    s_sensorfront_i <= sensor1_i;
                    sensor1_o <= s_sensorfront_o;

                    if(s_updatefront_i = '1') then
                        s_dist_lvl1 <= s_dist_lvl_front;
                        s_sensor_front <= RIGHT;
                    end if;

                when RIGHT =>
                    s_sensorfront_i <= sensor2_i;
                    sensor2_o <= s_sensorfront_o;

                    if(s_updatefront_i = '1') then
                        s_dist_lvl2 <= s_dist_lvl_front;
                        s_sensor_front <= LEFT;
                    end if;

                when others =>-- Other states
                    s_sensor_front <= LEFT;

            end case;
        end if;
    end if;
end if;
```

```

end process p_front_sensor_select;

-----
-- Proces for switching between Left & Center & Right back sensor
-- So only one is measuring at the moment
-----

p_back_sensor_select : process(clk)
begin
    if rising_edge(clk) then
        if (reset = '1') then
            s_sensor_back <= LEFT; -- Initial state
        else
            case s_sensor_back is

                when LEFT =>
                    s_sensorback_i <= sensor3_i;           -- Conecting input and output o
                    sensor3_o <= s_sensorback_o;           -- to its proper sensor input a

                    if(s_updateback_i = '1') then         -- Reciving update signal will.
                        s_dist_lv13 <= s_dist_lv1_back;   -- Save measured value to prope
                        s_sensor_back <= CENTER;           -- Change state.
                    end if;                                -- Rest works same, but with it

                when CENTER =>
                    s_sensorback_i <= sensor4_i;
                    sensor4_o <= s_sensorback_o;

                    if(s_updateback_i = '1') then
                        s_dist_lv14 <= s_dist_lv1_back;
                        s_sensor_back <= RIGHT;
                    end if;

                when RIGHT =>
                    s_sensorback_i <= sensor5_i;
                    sensor5_o <= s_sensorback_o;

                    if(s_updateback_i = '1') then
                        s_dist_lv15 <= s_dist_lv1_back;
                        s_sensor_back <= LEFT;
                    end if;

                when others =>-- Other states
                    s_sensor_back <= LEFT;

            end case;
        end if;
    end if;
end process p_back_sensor_select;

```

## B)VHDL design entities

There are 7 entities connected to parking assistant. We have 2 same entities `urm_driver_decoder` and 5 single entities `distance_comparator`, `beep_generator`, `mux_2bit_6to1`, `clock_enable`, `cnt_up_down`.

```

-----
-- Connecting entities to parking_assistant_6sensor
-----

-- Entity: Ultrasonic range meter driver - for front sensors
uut_urm_driver_front : entity work.urm_driver_decoder
    generic map(
        g_lvl_0      => g_distance_threshold1,
        g_lvl_1      => g_distance_threshold2,
        g_lvl_2      => g_distance_threshold3,
        g_lvl_3      => g_distance_threshold4
    )
    port map(
        clk           => clk,
        reset         => reset,
        sensor_out_i  => s_sensorfront_i,
        sensor_in_o   => s_sensorfront_o,
        dist_lvl_o    => s_dist_lvl_front,
        update_o      => s_updatefront_i
    );

-- Entity: Ultrasonic range meter driver - for back sensors
uut_urm_driver_back : entity work.urm_driver_decoder
    generic map(
        g_lvl_0      => g_distance_threshold1,
        g_lvl_1      => g_distance_threshold2,
        g_lvl_2      => g_distance_threshold3,
        g_lvl_3      => g_distance_threshold4
    )
    port map(
        clk           => clk,
        reset         => reset,
        sensor_out_i  => s_sensorback_i,
        sensor_in_o   => s_sensorback_o,
        dist_lvl_o    => s_dist_lvl_back,
        update_o      => s_updateback_i
    );

-- Entity: Comparation of distances measured by sensors
uut_distance_comparator : entity work.distance_comparator
    port map (
        a_i           => s_dist_lvl0,
        b_i           => s_dist_lvl1,
        c_i           => s_dist_lvl2,
        d_i           => s_dist_lvl3,
        e_i           => s_dist_lvl4,
        f_i           => s_dist_lvl5,
        greatest_o    => s_tone_gen_data_i
    );

-- Entity: For tone generation dependant on closest measuerd range
uut_tone_gen: entity work.beep_generator
    generic map(
        tone_freq     => g_tone_freq, -- 1000; --Hz
        slow_period   => g_slow_period, -- 5; --ms
        fast_period    => g_fast_period -- 2 --ms
    )

```

```

    port map (
        clk           => clk,
        reset         => reset,
        dist_lvl      => s_tone_gen_data_i,
        tone_o        => sound_o
    );

-- Entity: Multiplexer for 6-LEDs(bargraphs)
uut_mux_led: entity work.mux_2bit_6to1
    port map (
        a_i           => s_dist_lvl0,
        b_i           => s_dist_lvl1,
        c_i           => s_dist_lvl2,
        d_i           => s_dist_lvl3,
        e_i           => s_dist_lvl4,
        f_i           => s_dist_lvl5,
        sel_i         => s_sel_o,
        f_o           => LED_o
    );

-- Entity: For sending pulse every 2ms
uut_clk_en0 : entity work.clock_enable
    generic map(
        g_MAX         => 200000
    )
    port map(
        clk           => clk,
        reset         => reset,
        ce_o          => s_2ms
    );

-- Entity: To change multiplexer selector signal
uut_bin_cnt0 : entity work.cnt_up_down
    generic map(
        g_CNT_WIDTH  => 3
    )
    port map(
        clk           => clk,
        reset         => reset,
        en_i          => s_2ms,
        cnt_up_i      => '1',
        cnt_o         => s_sel_o
    );

    -- Connecting internal mux selecting singal to output
    sel_o <= s_sel_o;

end Behavioral;

```

### C)Testbench for parking assistant

There are 3 processes in testbench - p\_clk\_gen with frequency of 100MHz , p\_reset\_gen , p\_stimulus . Function of processes are displayed in simulations below.

---

```

-- Clock generation process

```

```

-----
p_clk_gen : process
begin
    while now < 100 ms loop
        s_clk <= '0';
        wait for c_CLK_100MHZ_PERIOD / 2;
        s_clk <= '1';
        wait for c_CLK_100MHZ_PERIOD / 2;
    end loop;
    wait;
end process p_clk_gen;

-----
-- Reset generation process
-----

p_reset_gen : process
begin

    -- Initial reset activated
    s_reset <= '1';
    wait for 100 us;

    -- Reset deactivated
    s_reset <= '0';
    wait for 3 ms;

    -- Reset activated
    s_reset <= '1';
    wait for 100 us;

    -- Reset deactivated
    s_reset <= '0';

    wait;
end process p_reset_gen;

-----
-- Data generation process
-----

p_stimulus : process
begin
    report "Stimulus process started" severity note;

    -- --1st block
    wait for 180 us;
    s_sensor0_out_i <= '1';
    s_sensor3_out_i <= '1';
    wait for c_dist_0;
    s_sensor0_out_i <= '0';
    s_sensor3_out_i <= '0';

    wait for 180 us;
    s_sensor1_out_i <= '1';
    s_sensor4_out_i <= '1';
    wait for c_dist_0;
    s_sensor1_out_i <= '0';
    s_sensor4_out_i <= '0';

```

```

wait for 100 us;
s_sensor2_out_i <= '1';
s_sensor5_out_i <= '1';
wait for c_dist_0;
s_sensor2_out_i <= '0';
s_sensor5_out_i <= '0';
--                                     --2nd block

wait for 180 us;
s_sensor0_out_i <= '1';
s_sensor3_out_i <= '1';
wait for c_dist_4;
s_sensor0_out_i <= '0';
s_sensor3_out_i <= '0';

wait for 180 us;
s_sensor1_out_i <= '1';
s_sensor4_out_i <= '1';
wait for c_dist_2;
s_sensor1_out_i <= '0';
s_sensor4_out_i <= '0';

wait for 100 us;
s_sensor2_out_i <= '1';
s_sensor5_out_i <= '1';
wait for c_dist_3;
s_sensor2_out_i <= '0';
s_sensor5_out_i <= '0';
--                                     --3rd block

wait for 180 us;
s_sensor0_out_i <= '1';
s_sensor3_out_i <= '1';
wait for c_dist_3;
s_sensor0_out_i <= '0';
s_sensor3_out_i <= '0';

wait for 180 us;
s_sensor1_out_i <= '1';
s_sensor4_out_i <= '1';
wait for c_dist_2;
s_sensor1_out_i <= '0';
s_sensor4_out_i <= '0';

wait for 100 us;
s_sensor2_out_i <= '1';
s_sensor5_out_i <= '1';
wait for c_dist_4;
s_sensor2_out_i <= '0';
s_sensor5_out_i <= '0';
--                                     --4th block

wait for 15 us;
s_sensor0_out_i <= '1';
s_sensor3_out_i <= '1';
wait for c_dist_5;
s_sensor0_out_i <= '0';
s_sensor3_out_i <= '0';

```



```

wait for 11 us;
s_sensor1_out_i <= '1';
s_sensor4_out_i <= '1';
wait for c_dist_5;
s_sensor1_out_i <= '0';
s_sensor4_out_i <= '0';


wait for 130 us;
s_sensor2_out_i <= '1';
s_sensor5_out_i <= '1';
wait for c_dist_5;
s_sensor2_out_i <= '0';
s_sensor5_out_i <= '0';

report "Stimulus process finished" severity note;
wait;
end process p_stimulus;


```
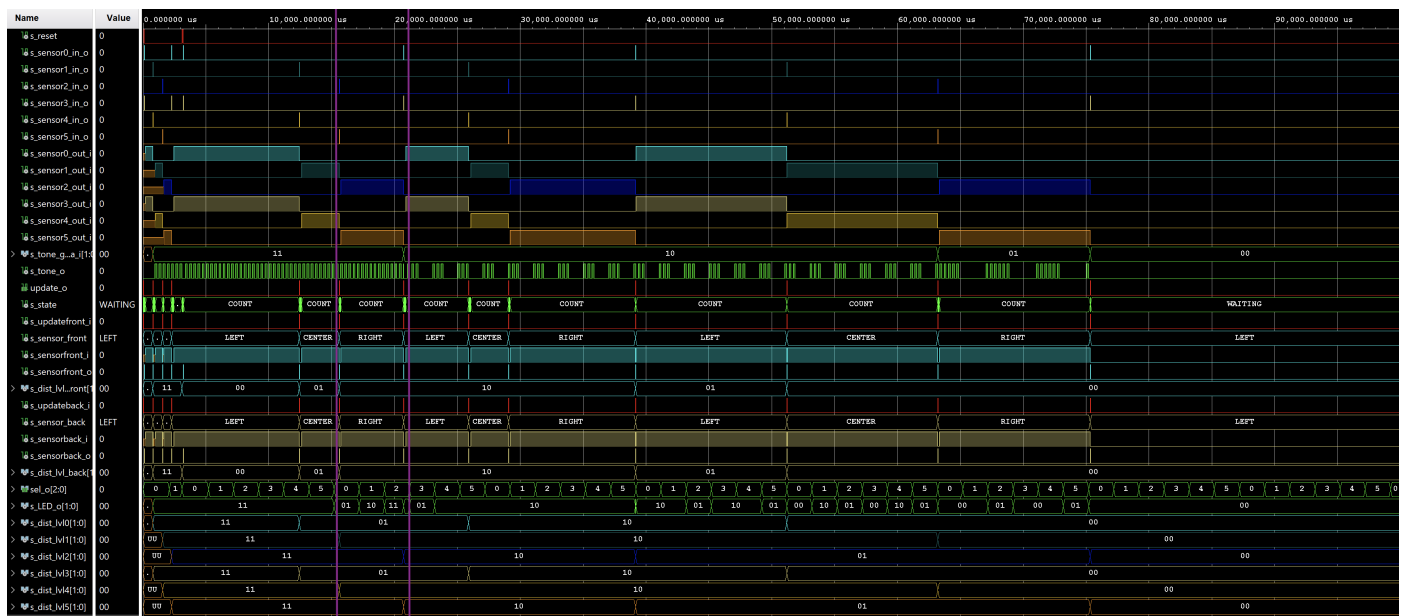
## D)Screenshots of simulation


In the first picture we can see the whole simulation. The signals with shades of blue are for front side, with shades of light brown are for back side, red signals represent updating internal signals that change state , green s\_tone signals represent sound output, green s\_state signal is internal signal of URM driver decoder and on last 2 green signals we can see LED output. Signals s\_sensor\_in\_o are sending 10us pulses to sensors and s\_sensor\_out\_i are receiving returning signals. From a short look we can tell that it works properly. The second and third picture is zoomed image of the first picture. The 1st zoomed area is marked with first violet vertical line and the 2nd zoomed area is marked with second violet vertical line. Signals s\_sensor2\_out\_i and s\_sensor5\_out\_i in this highlighted area are 5000us long, signals s\_sensor1\_out\_i and s\_sensor4\_out\_i are 3000us long. We will take a look at the zoomed pictures.




In the picture we can see ends of s\_sensor1\_out\_i and s\_sensor4\_out\_i signals which are 3000us long. After these signals change the state to 0, the update is triggered, every state changes to its right following position and the measured distance is saved to its proper value s\_dist\_lvl1 and s\_dist\_lvl4. With calculation we can check that 3000us long signal corresponds to 51cm which is above first treshold and this value is represented by 10 . After all that URM driver decoder sends 10us pulse into 2 following sensors and then waits for returning signal. At the end of this picture we can see returning signals (s\_sensor2\_out\_i and s\_sensor5\_out\_i) and we will take a look on the ends of these signals in the next picture.

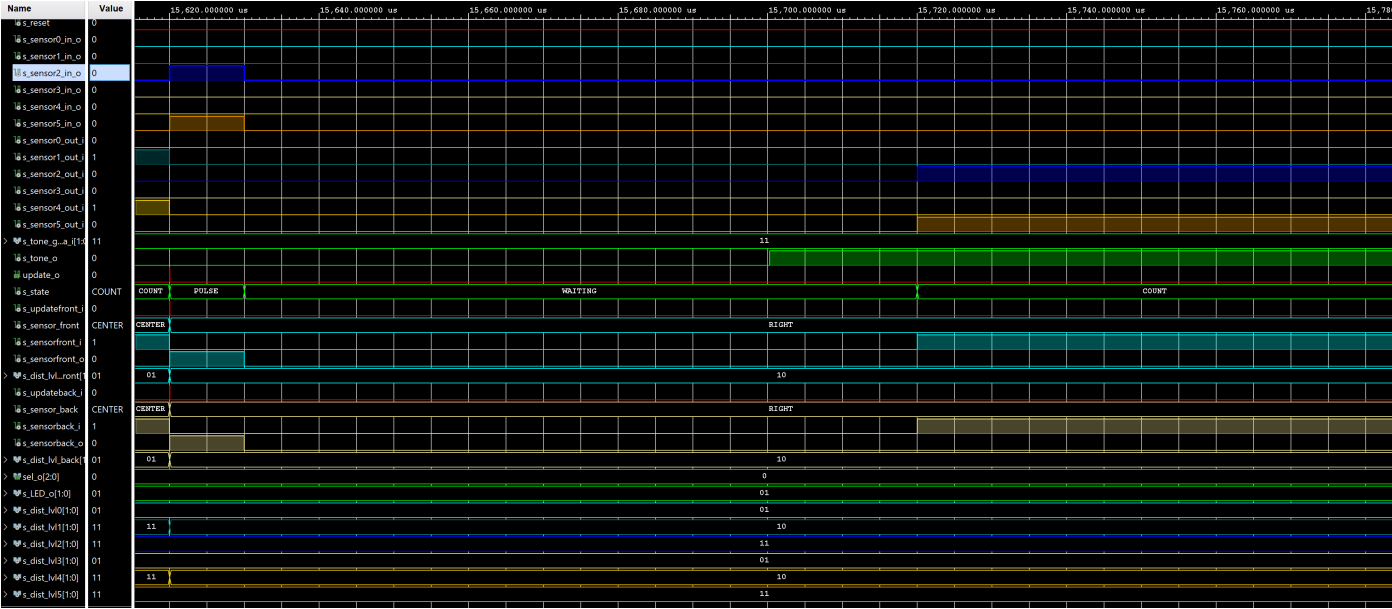

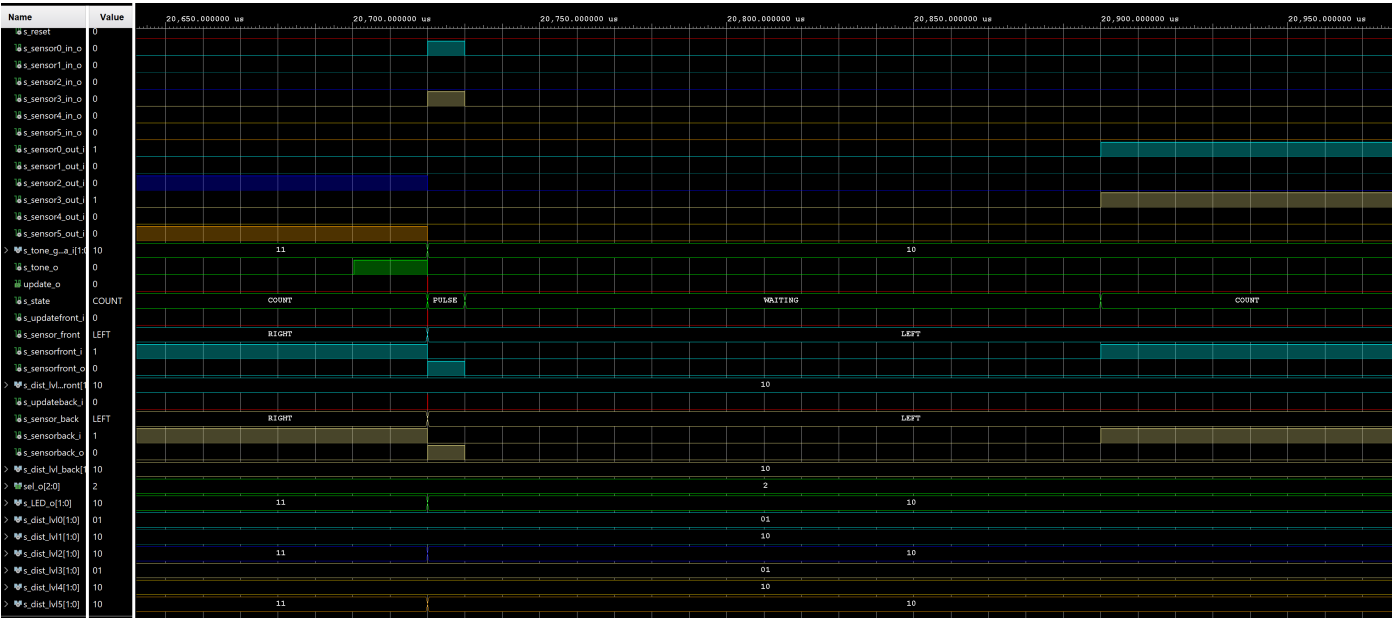In this picture it works the same like in simulation above but with s\_sensor2\_out\_i and s\_sensor5\_out\_i signals. The length of these signals are 5000us and it corresponds to 86cm which is again above first treshold and this value is represented by 10 .



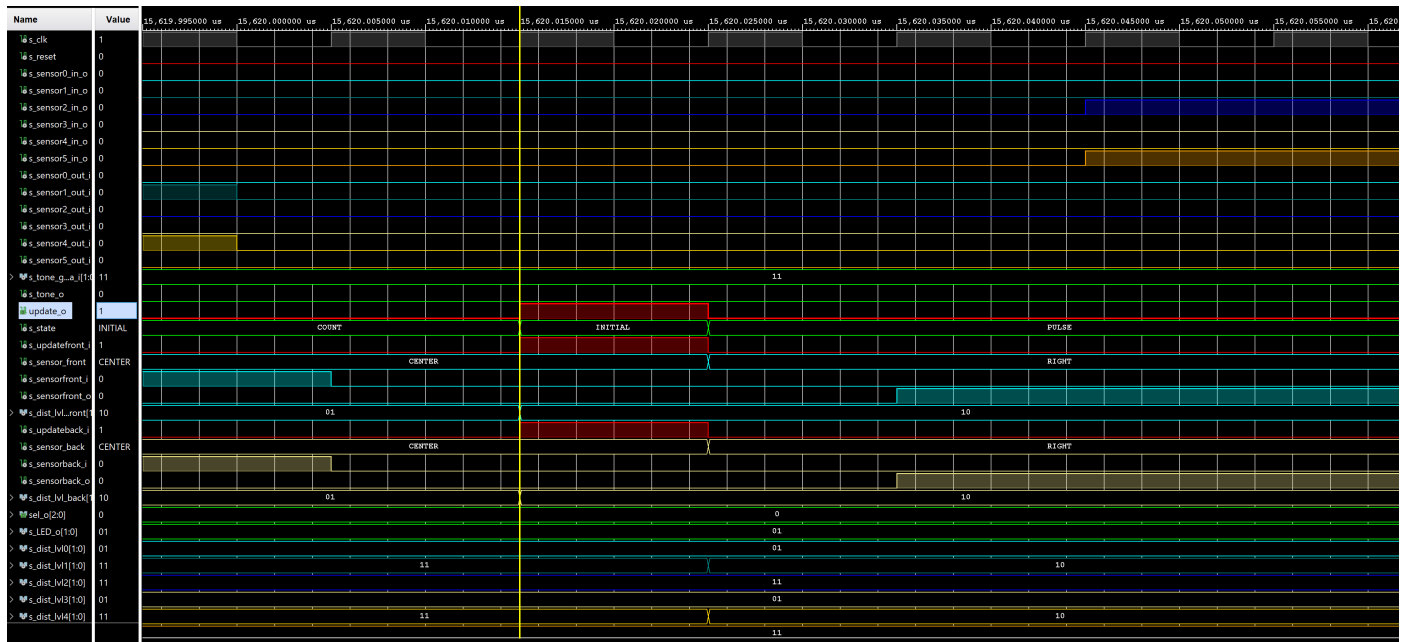This is close look on the update when it is triggered. And we can see that it works properly - it changes states to right positions.



Submodules of parking assistant :

## 2.URM (ultrasonic range meter) driver decoder

### A)VHDL design of URM driver decoder

Process for URM driver decoder. URM driver decoder communicates with each sensor separately. It sends 10us pulses, then waits for pulses coming back from the sensor. When it comes , it counts its length. After that, it assigns one of four tresholds to the output length measured.

```

-----
-- Process for sending 10us signal into a sensor &
-- For measuring returning signal
-----

p_distance_measurement : process(clk)
begin
    if rising_edge(clk) then
        if (reset = '1') then -- Synchronous reset
            s_state          <= INITIAL; -- Set initial state
            s_local_cnt      <= 0;       -- Clear all counters
            update_o         <= '0';    -- Reset update signal
            sensor_in_o      <= '0';    -- Reset sensor input
            s_distance       <= 201;    -- Initialize distance
        else
            case s_state is

                when INITIAL =>-- Initial state
                    if (reset = '0') then
                        s_state          <= PULSE;
                        update_o <= '0';-- Setting mux update to 0
                    end if;

                when PULSE =>-- State for sending 10us pulse
                    if (s_local_cnt >= (PULSE_LENGTH - 1)) then
                        s_local_cnt      <= 0; -- Clear counter
                        sensor_in_o      <= '0'; -- Reset output
                    end if;
            end case;
        end if;
    end if;
end process;

```

```

        s_state      <= WAITING;  -- Next state
    else -- 10 us counter
        s_local_cnt  <= s_local_cnt + 1;
        sensor_in_o  <= '1';
    end if;

    when WAITING =>-- Waiting state for signal returning from sensor
        if (sensor_out_i = '1') then
            s_state      <= COUNT;
        end if;

    when COUNT =>-- State for counting the length of returning signal
        if (sensor_out_i = '1') then -- Counter
            s_local_cnt  <= s_local_cnt + 1;
        else -- Dividing s_distance(length) of measured signal by constant 10
            s_distance    <= s_local_cnt /5800;    -- specified by datasheet
            s_local_cnt  <= 0;                    -- to eliminate effect of
            update_o      <= '1';                -- to get dist in cm.
            s_state      <= INITIAL;
        end if;

    when others =>-- Other states
        s_state <= INITIAL;

    end case;
end if;
end if;
end process p_distance_measurement;

-----
-- Process for quantization measured signal
-----
p_dist_decoder : process(s_distance)
begin
    if (s_distance <= g_lvl_0) then -- The closest distance
        dist_lvl_o <= "11";
    elsif(s_distance <= g_lvl_1) then
        dist_lvl_o <= "10";
    elsif(s_distance <= g_lvl_2) then
        dist_lvl_o <= "01";
    else
        dist_lvl_o <= "00"; -- The furthest distance
    end if;
end process p_dist_decoder;

```

## B)Testbench

In testbench we simulate signals which are coming back.

```

-----
-- Clock generation process
-----
p_clk_gen : process
begin

```

```

while now < 750 ms loop
    s_clk <= '0';
    wait for c_CLK_100MHZ_PERIOD / 2;
    s_clk <= '1';
    wait for c_CLK_100MHZ_PERIOD / 2;
end loop;
wait;                                -- Process is suspended forever
end process p_clk_gen;

-----
-- Reset generation process
-----

p_reset_gen : process
begin

    --Initial reset activated
    s_reset <= '1';
    wait for 100 us;

    -- Reset deactivated
    s_reset <= '0';

    wait;
end process p_reset_gen;


-----
-- Data generation process
-----

p_stimulus : process
begin
    report "Stimulus process started" severity note;
    wait for 500 us;                -- Waiting for initial pulse
    s_sensor_out_i <= '1';
    wait for 150 us;                -- "Receiving" distance lesser than lvl_0 distance
    s_sensor_out_i <= '0';          -- its length is 2.58 cm (150/58)
    wait for 50 us;                -- Waiting for sending 10us pulse (We have to wait
    s_sensor_out_i <= '1';          -- at least 10us. Here we wait 50us to be sure.)
    wait for 3000 us;              -- "Receiving" distance bigger than lvl_0 distance
    s_sensor_out_i <= '0';          -- its length is 51.8 cm (3000/58)
    wait for 50 us;                -- Waiting for sending 10us pulse
    s_sensor_out_i <= '1';
    wait for 6000 us;              -- "Receiving" distance bigger than lvl_1 distance
    s_sensor_out_i <= '0';          -- its length is 103.4 cm (6000/58)
    wait for 50 us;                -- Waiting for sending 10us pulse
    s_sensor_out_i <= '1';
    wait for 12000 us;             -- "Receiving" distance bigger than lvl_2 distance
    s_sensor_out_i <= '0';          -- its length is 206.9 cm (12000/58)
    wait for 50 us;                -- Waiting for sending 10us pulse
    s_sensor_out_i <= '1';
    wait for 24000 us;             -- "Receiving" distance bigger than lvl_2 distance
    s_sensor_out_i <= '0';          -- its length is 413.8 cm (24000/58)
    wait for 50 us;
    report "Stimulus process finished" severity note;
    wait;
end process p_stimulus;

```
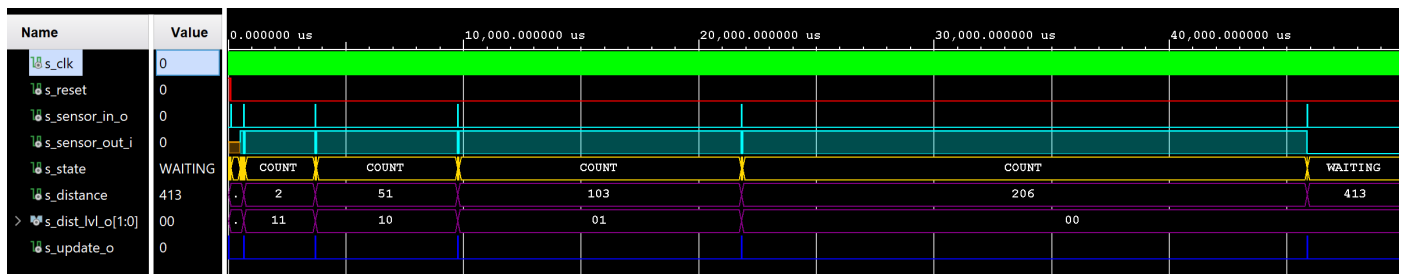
## C) Screenshots of simulation


The first picture is a look on the whole simulation which is 50ms long. Again from a short look we can see that it works properly.




In the zoomed picture we can find the ending of returning signal which is then added to s\_dist\_lvl\_o. After that the update is triggered and the new cycle starts again.



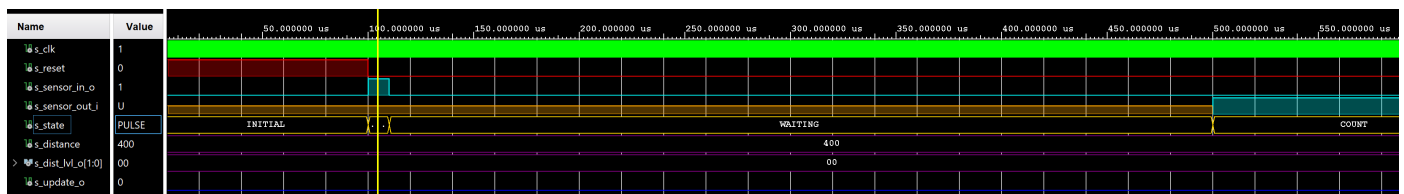Here we can see the beginning of this simulation when the reset is on (it is in value of 1). When the reset is in value of 0 then the whole cycle starts ( Initial --> Pulse --> Waiting --> Count --> Initial...).



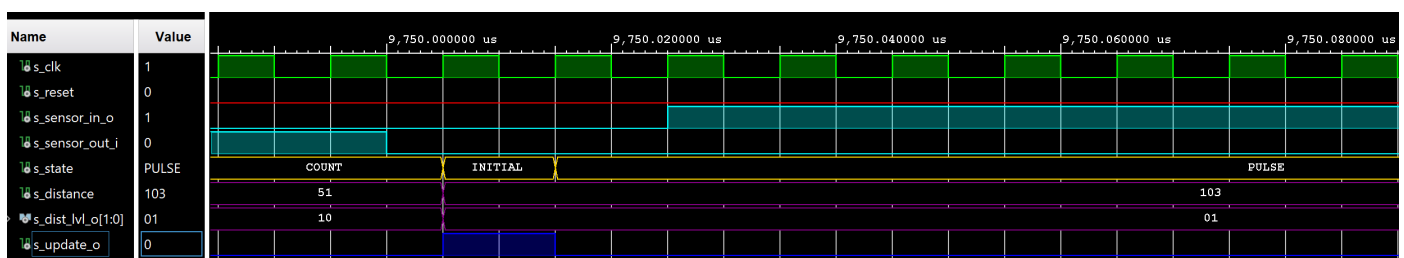Here we can see the proper function of update.



## 3.Beep generator

### A)VHDL design

This process describes changing frequency of the tone based on distance change. When the distance is shortest the sound creates continuous tone, the second shortest distance generates fast beeping. The bigger is distance , the slower are sounds of beeping. We can hear nothing when the distance is too far.

```

-----
-- Process for changing frequency of the tone
-----
p_pulse_clock : process(pulse_clock_period,clk) -- Generates signal, which determines
begin                                           -- frequency of beeping.
    if (rising_edge(clk)) then
        if (s_pulse_counter < 100000*pulse_clock_period) then
            s_pulse_counter <= s_pulse_counter +1;
        else
            pc_out <= not pc_out;
            s_pulse_counter <= 0;
        end if;
    end if;
end process p_pulse_clock;

-----
-- Process for changing frequency of tone depending on the input
-----
p_clock_enable : process(dist_lvl,clk)
begin
    case dist_lvl is
        when "11" => -- Shortest distance => continuous tone
            s_en <= '1'; -- Tone generator output enabled
        when "10" => -- Second shortest distance => fast bee
            pulse_clock_period <= fast_period; -- Pulse clock generates fast beeping s
            s_en <= pc_out; -- Enables tone generator output with t
        when "01" => -- Second longest distance => slow beep
            pulse_clock_period <= slow_period; -- Pulse clock generates slow beeping s
            s_en <= pc_out; -- Enables tone generator output with t
        when others => -- Farthest distance => silence
            s_en <= '0'; -- Tone generator output off
    end case;
end process p_clock_enable;

-----
-- Tone generating process
-----
p_1kHz_gen : process(clk, s_en) -- Tone generator
begin
    if rising_edge(clk) then
        if (reset = '1') then
            s_clk_counter <= 0;
            s_local_clock <= '0';
            tone_o <= '0';
        elsif (s_clk_counter >= ((s_clk_period-1)/2 )) then
            s_clk_counter <= 0;
            s_local_clock <= not s_local_clock;
        else
            s_clk_counter <= s_clk_counter + 1;
        end if;
    end if;

    if (s_en = '1') then
        tone_o <= s_local_clock; -- Enables tone gen. output
    else
        tone_o <= '0';
    end if;
end process p_1kHz_gen;

```

```

        end if;
    end process p_1kHz_gen;

```

## B) Testbench

```

-----
-- Reset generation process
-----
p_clk_gen : process
begin
    while now < 50 ms loop
        s_clk_100MHz <= '0';
        wait for c_CLK_100MHz_PERIOD / 2;
        s_clk_100MHz <= '1';
        wait for c_CLK_100MHz_PERIOD / 2;
    end loop;
    wait;
end process p_clk_gen;

-----
-- Data generation process
-----
p_stimulus : process
begin
    report "Stimulus process started" severity note;


    distance_lvl <= "00";
    wait for 10ms;
    distance_lvl <= "01";
    wait for 10ms;
    distance_lvl <= "10";
    wait for 10ms;
    distance_lvl <= "11";

    report "Stimulus process finished" severity note;
    wait;
end process p_stimulus;

```
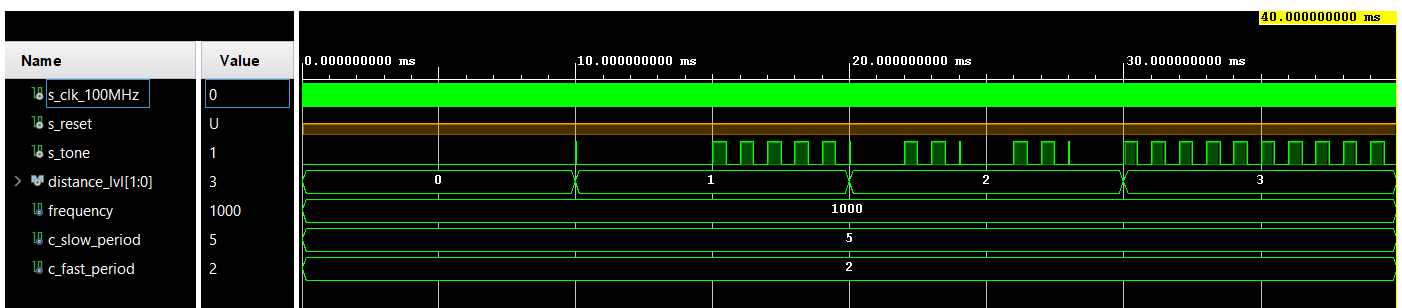
## C) Screenshot of simulation

When the distance changes period of beeping signal is changed. As displayed on simulation below





## 4. Distance comparator

This entity compares measured distances, and returns the closest distance measured - in our project it is defined that in bit it means that it is the highest value.

### A)VHDL design

```
-----  
-- Process for finding highest value  
-----  
p_comp : process(a_i,b_i,c_i,d_i,e_i,f_i,temp_1,temp_2,temp_3,temp_4)  
begin  
    -- Finding the highest value from input signals, saving them into temporary signals  
    if (b_i >= a_i) then  
        temp_1 <= b_i;  
    else  
        temp_1 <= a_i;  
    end if;  
  
    if (c_i >= d_i) then  
        temp_2 <= c_i;  
    else  
        temp_2 <= d_i;  
    end if;  
  
    if (e_i >= f_i) then  
        temp_3 <= e_i;  
    else  
        temp_3 <= f_i;  
    end if;  
  
    -- Finding the highest value of the temporary signals.  
    if (temp_1 >= temp_2) then  
        temp_4 <= temp_1;  
    else  
        temp_4 <= temp_2;  
    end if;  
  
    -- Greatest value sent to output.  
    if (temp_4 >= temp_3) then  
        greatest_o <= temp_4;  
    else  
        greatest_o <= temp_3;  
    end if;  
end process p_comp;
```

### B) Testbench

```
-- Connecting testbench signals with distance_comparator  
uut_distance_comparator : entity work.distance_comparator  
    port map(  
        a_i          => s_a,  
        b_i          => s_b,
```

```

        c_i          => s_c,
        d_i          => s_d,
        e_i          => s_e,
        f_i          => s_f,
        greatest_o    => s_goat
    );

```

```

-----
-- Data generation process
-----

```

```

p_stimulus : process
begin
    report "Stimulus process started" severity note;
    s_a <= "01";
    s_b <= "00";
    s_c <= "00";
    s_d <= "00";
    s_e <= "00";
    s_f <= "00";
    wait for 10ns;

    s_a <= "00";
    s_b <= "01";
    s_c <= "00";
    s_d <= "00";
    s_e <= "00";
    s_f <= "00";
    wait for 10ns;

    s_a <= "00";
    s_b <= "00";
    s_c <= "01";
    s_d <= "00";
    s_e <= "00";
    s_f <= "00";
    wait for 10ns;

    s_a <= "00";
    s_b <= "00";
    s_c <= "00";
    s_d <= "01";
    s_e <= "00";
    s_f <= "00";
    wait for 10ns;

    s_a <= "00";
    s_b <= "00";
    s_c <= "00";
    s_d <= "01";
    s_e <= "00";
    s_f <= "00";
    wait for 10ns;

    s_a <= "00";
    s_b <= "00";
    s_c <= "00";
    s_d <= "00";
    s_e <= "01";

```

```

s_f <= "00";
wait for 10ns;


s_a <= "00";
s_b <= "00";
s_c <= "00";
s_d <= "00";
s_e <= "00";
s_f <= "01";
wait for 10ns;

s_a <= "11";
s_b <= "11";
s_c <= "00";
s_d <= "00";
s_e <= "00";
s_f <= "01";
wait for 10ns;
wait;
end process p_stimulus;

```
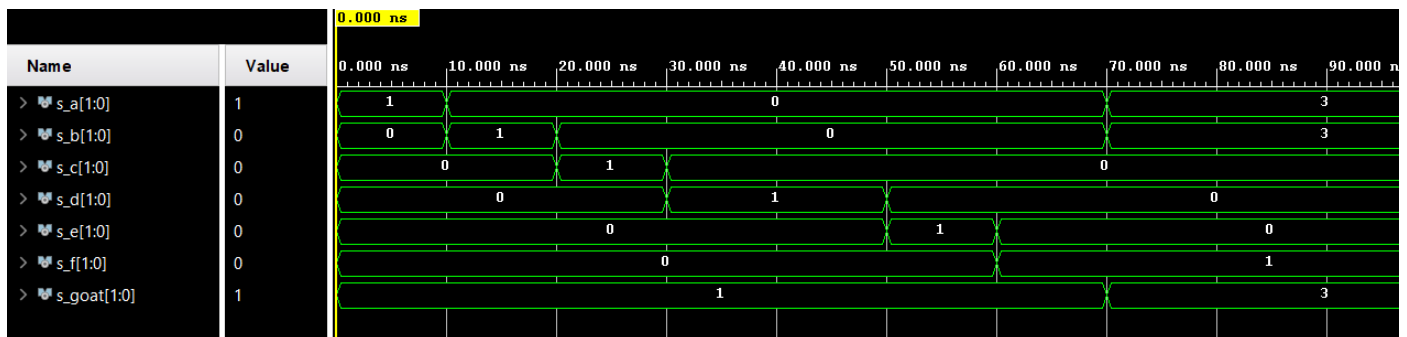
### C) Screenshot of simulation

On the image below we can see that input values can be different but the entity always return one, that is greatest = s\_goat.



## 5. cnt\_up\_down

One of the two entities that were made in school. It works the same but it was a bit modified. It only counts to value b"101" - 5 and then it resets itself.

### A) VHDL design

```

-----
-- p_cnt_up_down:
-- Clocked process with synchronous reset which implements n-bit
-- up/down counter.
-----

```

```

p_cnt_up_down : process(clk)
begin
    if rising_edge(clk) then

        if (reset = '1') then                -- Synchronous reset
            s_cnt_local <= (others => '0'); -- Clear all bits

```

```

        elsif (en_i = '1') then          -- Test if counter is enabled
            if (cnt_up_i = '1') then
                if (s_cnt_local >= b"101") then    -- Counter Shortened to 6 values
                    s_cnt_local <= b"000";
                else
                    s_cnt_local <= s_cnt_local + 1;
                end if;
            else
                s_cnt_local <= s_cnt_local - 1;
            end if;
        end if;
    end if;
end process p_cnt_up_down;

-- Output must be retyped from "unsigned" to "std_logic_vector"
cnt_o <= std_logic_vector(s_cnt_local);

```

## B) Testbench

```

-----
-- Clock generation process
-----
p_clk_gen : process
begin
    while now < 750 ns loop          -- 75 periods of 100MHz clock
        s_clk_100MHz <= '0';
        wait for c_CLK_100MHZ_PERIOD / 2;
        s_clk_100MHz <= '1';
        wait for c_CLK_100MHZ_PERIOD / 2;
    end loop;
    wait;
end process p_clk_gen;

-----
-- Reset generation process
-----
p_reset_gen : process
begin

    -- Reset activated
    s_reset <= '1';
    wait for 50 ns;

    s_reset <= '0';
    wait;
end process p_reset_gen;

-----
-- Data generation process
-----
p_stimulus : process
begin
    report "Stimulus process started" severity note;


```

```
-- Enable counting
s_en      <= '1';
s_cnt_up <= '1';
wait for 380 ns;
-- Disable counting
s_en      <= '0';

report "Stimulus process finished" severity note;
wait;
```
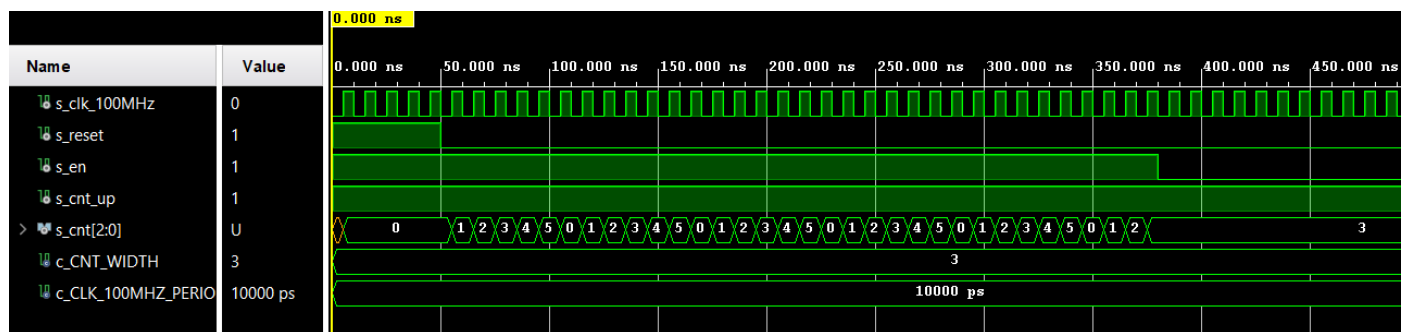
### C) Screenshot of simulation

On this simulation image we can see that it counts properly, when the enabling (s\_en) signal is positive, from zero to number five, and then it resets itself.



## 6. mux\_2bit\_6to1

We use this VHDL design from entity which we made at seminar at school but it was also a little bit modified.

## A)VHDL design

```
architecture Behavioral of mux_2bit_6to1 is

begin

    f_o <= a_i when (sel_i = "000") else
           b_i when (sel_i = "001") else
           c_i when (sel_i = "010") else
           d_i when (sel_i = "011") else
           e_i when (sel_i = "100") else
           f_i;

end Behavioral;
```

## B) Testbench

```
-- Data generation process
```

```


report "Stimulus process started" severity note;
s_a <= "00";
s_b <= "01";
s_c <= "10";
s_d <= "11";
s_e <= "00";
s_f <= "01";

s_sel <= "000";
wait for 10ns;
s_sel <= "001";
wait for 10ns;
s_sel <= "010";
wait for 10ns;
s_sel <= "011";
wait for 10ns;
s_sel <= "100";
wait for 10ns;
s_sel <= "101";

wait;
end process p_stimulus;

```

### C) Screenshot of simulation

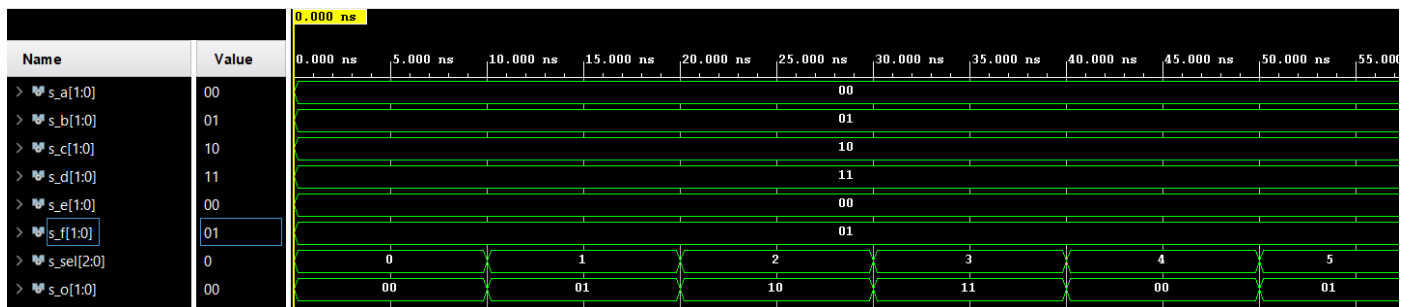

## TOP module description and simulations

TOP module is designed for connecting code signal to pins of Arty-A7-100 but it is same as the parking assistant.

### A) VHDL design

```

-- Connecting testbench signals with beep_generator
uut_parking_assistant : entity work.parking_assistant_6sensor
generic map(

    -- Optionable constants
    g_tone_freq    => 1000,
    g_slow_period  => 5,
    g_fast_period  => 2,

    -- Thresholds of measured distances
    g_distance_threshold1 => 50,
    g_distance_threshold2 => 150,

```

```

g_distance_threshold3 => 250,
g_distance_threshold4 => 400
)
port map (
    -- Clk & Reset signal
    clk      => CLK100MHZ,
    reset    => BTN(0),

    -- Inputs from sensors
    sensor0_i => JB(0),
    sensor1_i => JB(1),
    sensor2_i => JB(2),
    sensor3_i => JB(3),
    sensor4_i => JB(4),
    sensor5_i => JB(5),

    -- Outputs to sensors
    sensor0_o => JC(0),
    sensor1_o => JC(1),
    sensor2_o => JC(2),
    sensor3_o => JC(3),
    sensor4_o => JC(4),
    sensor5_o => JC(5),

    -- LEDs output & and their mux selector output
    LED_o(0)  => JA(0),
    LED_o(1)  => JA(1),
    sel_o(0)  => JA(2),
    sel_o(1)  => JA(3),
    sel_o(2)  => JA(4),

    -- Sound output
    sound_o   => JA(5)
);

```

## Logical circuit to decode LED outputs

---

These selecting signal sel\_i are switching between individual bargraphs and signals LED\_o determine which LEDs will be on. We will connect output pins of our board to this logical function.





We used this reference manual to find out how the sensors work...

[Reference manual](https://www.gie.com.my/download/um/modules/sensor/um_hc_sr04.pdf) - [https://www.gie.com.my/download/um/modules/sensor/um\\_hc\\_sr04.pdf](https://www.gie.com.my/download/um/modules/sensor/um_hc_sr04.pdf)

And to be sure we watched first few minutes of this video where the man explains how to sensor work in details.

[Explaining ultrasonic sensor](https://www.youtube.com/watch?v=6F1B_N6LuKw&t=100s) - [https://www.youtube.com/watch?v=6F1B\\_N6LuKw&t=100s](https://www.youtube.com/watch?v=6F1B_N6LuKw&t=100s)