



Learn Git and GitHub without any code!

Using the Hello World guide, you'll start a branch, write comments, and open a pull request.

Read the guide

SimonCieslar / Digital-electronics-1

MIT License

0 stars 1 fork

☆ Star

👁 Unwatch ▼

<> Code

🔔 Issues

🔗 Pull requests

▶ Actions

📁 Projects

📖 Wiki

🛡 Security

📈 Insights

main ▼

...

Digital-electronics-1 / Labs / 04-segment / README.md

SimonCieslar Update README.md 🕒 History

1 contributor

RawBlame

202 lines (154 sloc) | 6.71 KB

Labs - 04 - Segment

Lab assignment

1. Preparation tasks (done before the lab at home). Submit:
 - Figure or table with connection of 7-segment displays on Nexys A7 board,

- Decoder truth table for common anode 7-segment display.

2. Seven-segment display decoder. Submit:


- Listing of VHDL architecture from source file `hex_7seg.vhd` with syntax highlighting,
- Listing of VHDL stimulus process from testbench file `tb_hex_7seg.vhd` with syntax highlighting and asserts,
- Screenshot with simulated time waveforms; always display all inputs and outputs,
- Listing of VHDL code from source file `top.vhd` with 7-segment module instantiation.

3. LED(7:4) indicators. Submit:

- Truth table and listing of VHDL code for LEDs(7:4) with syntax highlighting,
- Screenshot with simulated time waveforms; always display all inputs and outputs.

1. Preparation tasks (done before the lab at home).

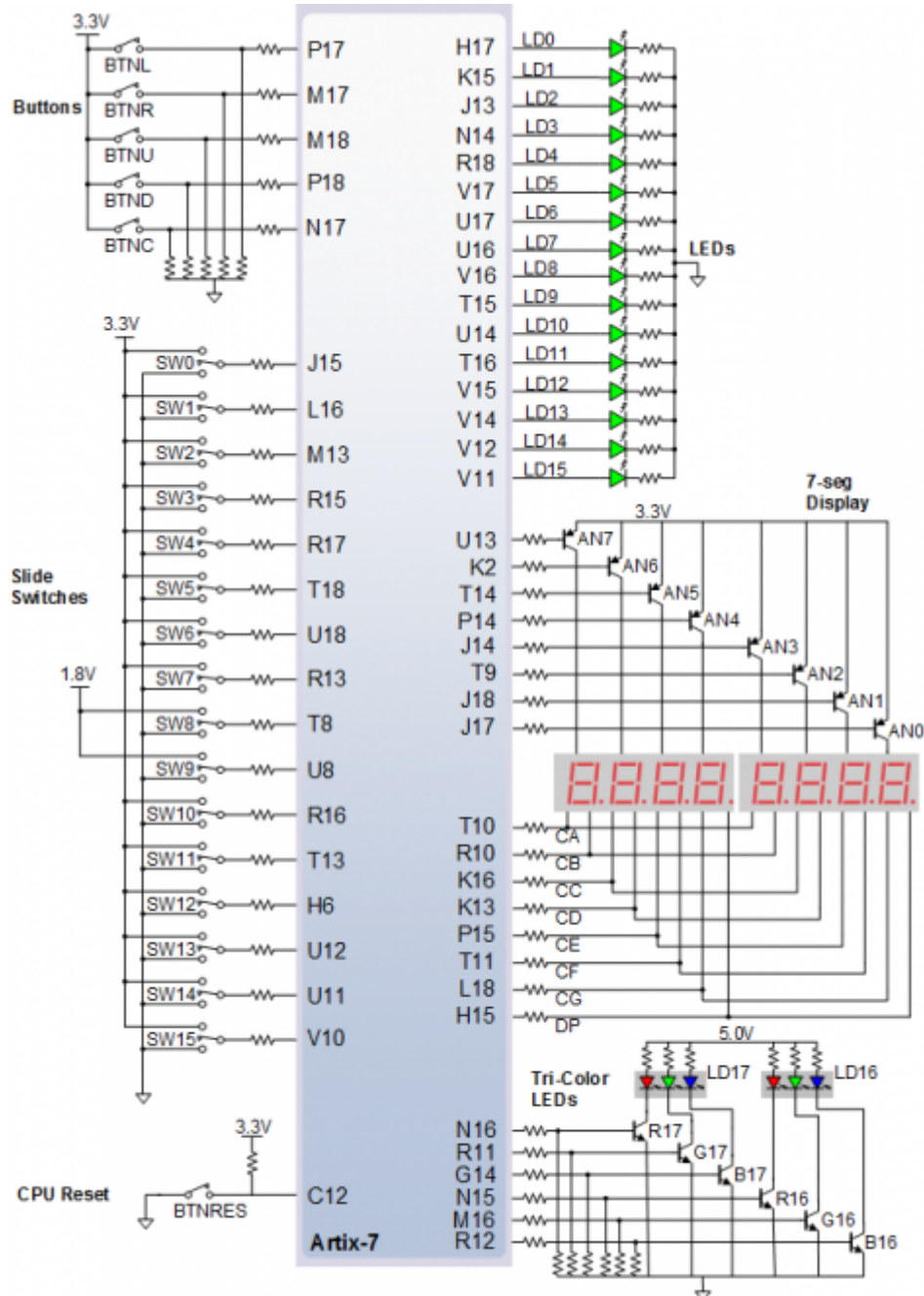1.1. Figure or table with connection of 7-segment displays on Nexys A7 board




1.2. Decoder truth table for common anode 7-segment display

Hex	Input	A	B	C	D	E	F	G
0	0000	0	0	0	0	0	0	1
1	0001	1	0	0	1	1	1	1
2	0010	0	0	1	0	0	1	0
3	0011	0	0	0	0	1	1	0
4	0100	1	0	0	1	1	0	0
5	0101	0	1	0	0	1	0	0
6	0110	0	1	0	0	0	0	0

Hex	Input	A	B	C	D	E	F	G
7	0111	0	0	0	1	1	1	1
8	1000	0	0	0	0	0	0	0
9	1001	0	0	0	0	1	0	0
A	1010	0	0	0	1	0	0	0
b	1011	1	1	0	0	0	0	0
C	1100	0	1	1	0	0	0	1
d	1101	1	0	0	0	0	1	0
E	1110	0	1	1	0	0	0	0
F	1111	0	1	1	1	0	0	0

 7 Segment formulation numbers and letters



2. Seven-segment display decoder.

2.1. Listing of VHDL architecture from source file `hex_7seg.vhd` with syntax highlighting

```

p_7seg_decoder : process(hex_i)
begin
    case hex_i is
        when "0000" =>
            seg_o <= "0000001"; -- 0
        when "0001" =>
            seg_o <= "1001111"; -- 1
        when "0010" =>
            seg_o <= "0010010"; -- 2
        when "0011" =>
            seg_o <= "0000110"; -- 3
        when "0100" =>
            seg_o <= "1001100"; -- 4
        when "0101" =>
            seg_o <= "0100100"; -- 5
    end case;
end process;

```

```

        when "0110" =>
            seg_o <= "0100000";      -- 6
        when "0111" =>
            seg_o <= "0001111";      -- 7
        when "1000" =>
            seg_o <= "0000000";      -- 8
        when "1001" =>
            seg_o <= "0000100";      -- 9
        when "1010" =>
            seg_o <= "0001000";      -- A
        when "1011" =>
            seg_o <= "1100000";      -- B
        when "1100" =>
            seg_o <= "0110001";      -- C
        when "1101" =>
            seg_o <= "1000010";      -- D
        when "1110" =>
            seg_o <= "0110000";      -- E
        when others =>
            seg_o <= "0111000";      -- F
    end case;
end process p_7seg_decoder;

```

2.2. Listing of VHDL stimulus process from testbench file `tb_hex_7seg.vhd` with syntax highlighting and asserts

```

p_stimulus : process
begin
    report "Stimulus process started" severity note;

    s_hex <= "0000"; wait for 100 ns;

    s_hex <= "0001"; wait for 100 ns;

    s_hex <= "0010"; wait for 100 ns;

    s_hex <= "0011"; wait for 100 ns;

    s_hex <= "0100"; wait for 100 ns;

    s_hex <= "0101"; wait for 100 ns;

    s_hex <= "0110"; wait for 100 ns;

    s_hex <= "0111"; wait for 100 ns;

    s_hex <= "1000"; wait for 100 ns;

    s_hex <= "1001"; wait for 100 ns;

    s_hex <= "1010"; wait for 100 ns;

    s_hex <= "1011"; wait for 100 ns;

```

```

s_hex <= "1100"; wait for 100 ns;

s_hex <= "1101"; wait for 100 ns;


s_hex <= "1110"; wait for 100 ns;

s_hex <= "1111"; wait for 100 ns;

report "Stimulus process finished" severity note;
wait;
end process p_stimulus;

```

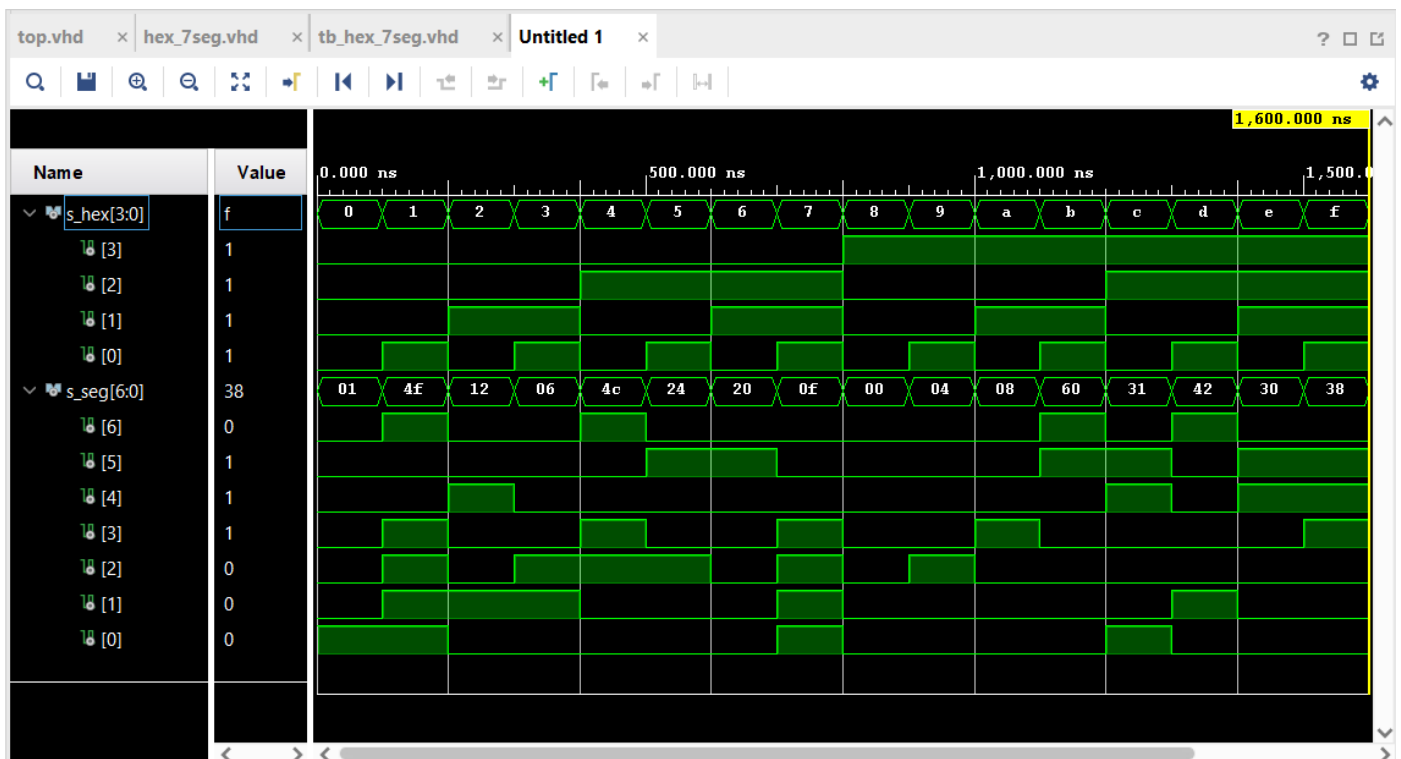2.3. Screenshot with simulated time waveforms; always display all inputs and outputs



2.4. Listing of VHDL code from source file `top.vhd` with 7-segment module instantiation

```

hex2seg : entity work.hex_7seg
port map(
    hex_i    => SW,
    seg_o(6) => CA,
    seg_o(5) => CB,
    seg_o(4) => CC,
    seg_o(3) => CD,
    seg_o(2) => CE,
    seg_o(1) => CF,
    seg_o(0) => CG
);

```

3. LED(7:4) indicators.

3.1. Truth table and listing of VHDL code for LEDs(7:4) with syntax highlighting

Hex	Inputs	LED4	LED5	LED6	LED7
0	0000	1	0	0	0
1	0001	0	0	1	1
2	0010	0	0	0	1
3	0011	0	0	1	0
4	0100	0	0	0	1
5	0101	0	0	1	0
6	0110	0	0	0	0
7	0111	0	0	1	0
8	1000	0	0	0	1
9	1001	0	0	1	0
A	1010	0	1	0	0
b	1011	0	1	1	0
C	1100	0	1	0	0
d	1101	0	1	1	0
E	1110	0	1	0	0
F	1111	0	1	1	0

```
-- Display input value
LED(3 downto 0) <= SW;

-- Turn LED(4) on if input value is equal to 0, ie "0000"
LED(4) <= '1' when (SW = "0000") else '0';

-- Turn LED(5) on if input value is greater than "1001"
LED(5) <= '1' when (SW > "1001") else '0';

-- Turn LED(6) on if input value is odd, ie 1, 3, 5, ...
LED(6) <= '1' when (SW = "0001" or SW = "0011" or SW = "0101" or SW = "0111" or SW = "1001" or SW = "1011" or SW = "1101" or SW = "1111") else '0';

-- Turn LED(7) on if input value is a power of two, ie 1, 2, 4, or 8
LED(7) <= '1' when (SW = "0001" or SW = "0010" or SW = "0100" or SW = "1000") else '0';
end Behavioral;
```

3.2. Screenshot with simulated time waveforms; always display all inputs and outputs

